

## **CS -268 | MIDSEM REPORT FILE**

Submitted By -


Pradumya Gaurav | ID – 202251096

Sourabh Ramakrishna Patil | ID – 202251095

Malaika Varshney | ID - 202251069

Submitted To - Dr. Kamal Kishore Jha

# CS - 268 | Lab Report

 


## Report File | Week - 01

## Question:

Designing of 1-bit and 4-bit ALU using Logisim.
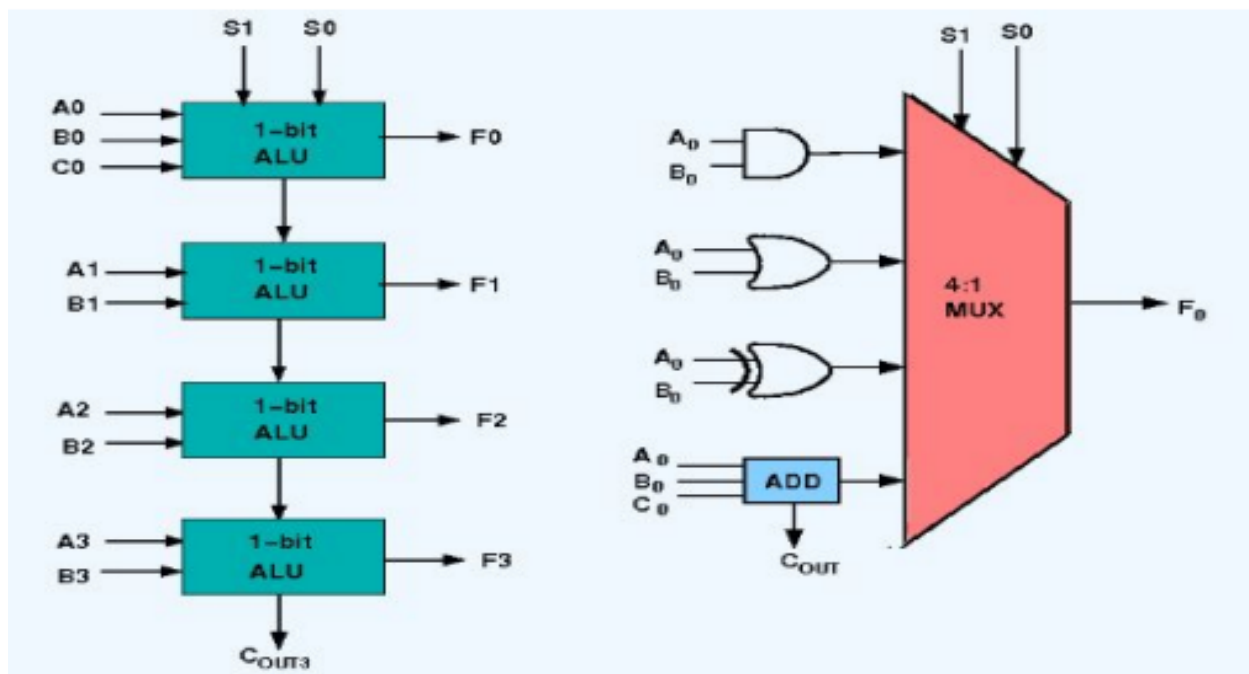
## Theory:


ALU or Arithmetic Logical Unit is a digital circuit to do arithmetic operations like addition, subtraction, division, multiplication and logical operations like and, or, xor, nand, nor etc. A simple block diagram of a 4 bit ALU for operations and, or, xor and Add is shown here .




## Design & Procedure:

The figure shown below depicts 1-bit ALU. It performs 8 operations :

 
1. AND Operation
2. OR Operation
3. XOR Operation
4. NOR Operation
5. GREATER THAN Comparator
6. EQUAL TO Comparator
7. LESSER THAN Comparator
8. ADDER/SUBTRACTOR Operation



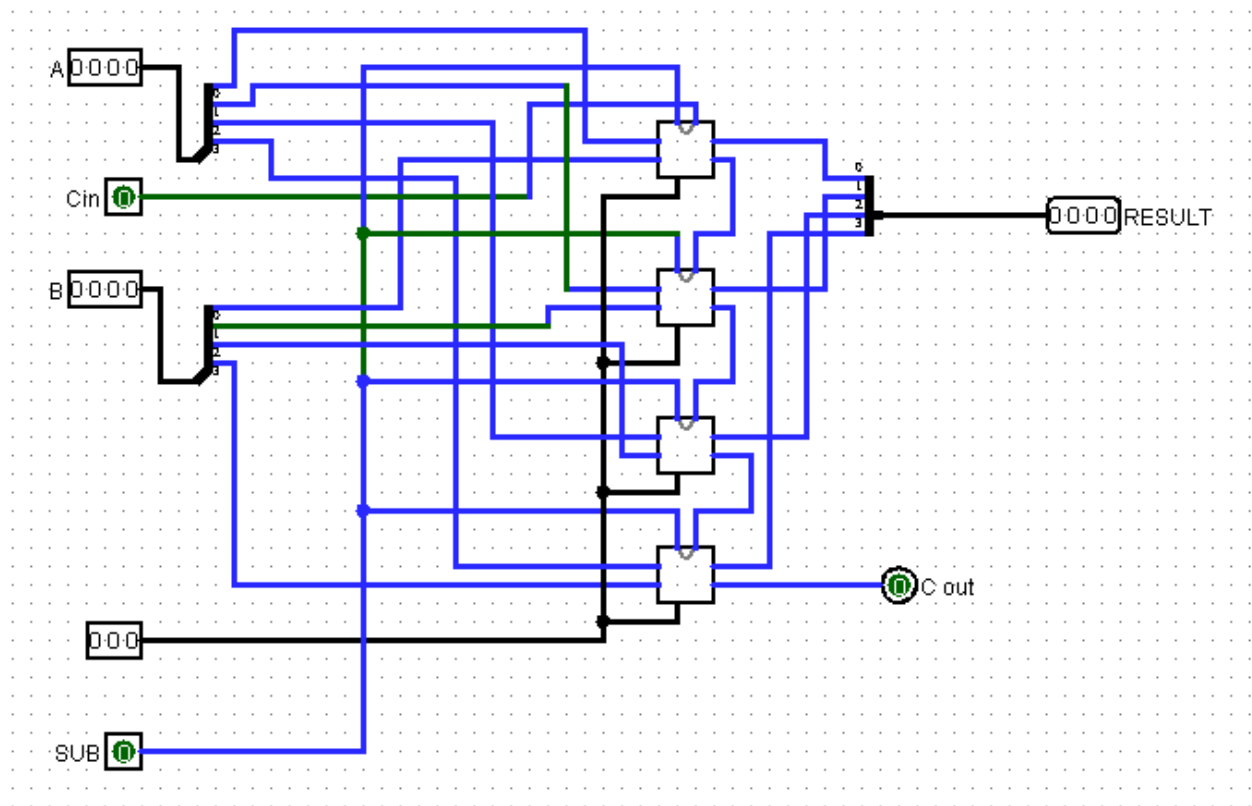With the help of 1-bit ALU, we constructed a 4-bit ALU where carry/borrow propagates from 1st 1-bit ALU to others. Below is the figure of 4-bit ALU.



## Testing of 1-bit ALU:

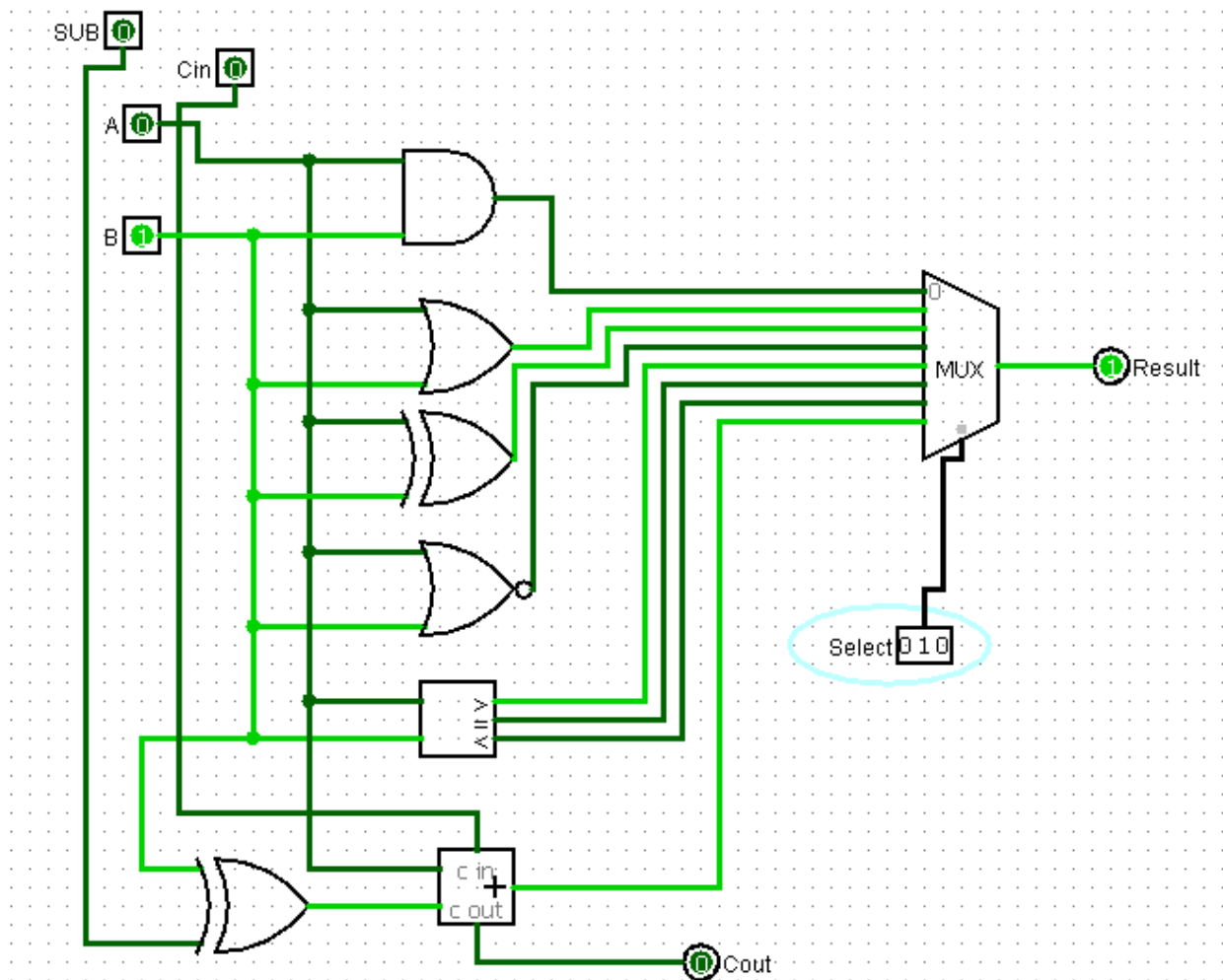


- First, we will choose the select line in 8:1 MUX. Then, we will provide inputs in A and B and finally the result gets displayed based on the select line chosen by the user.
- In the above example, select line chosen is 010 i.e, XOR Operator.



- By providing the input in A and B as 0 and 1 respectively we get the result as 1.
- Similarly, we can perform other operations too.

## Testing of 4-bit ALU:


### XOR Operation:

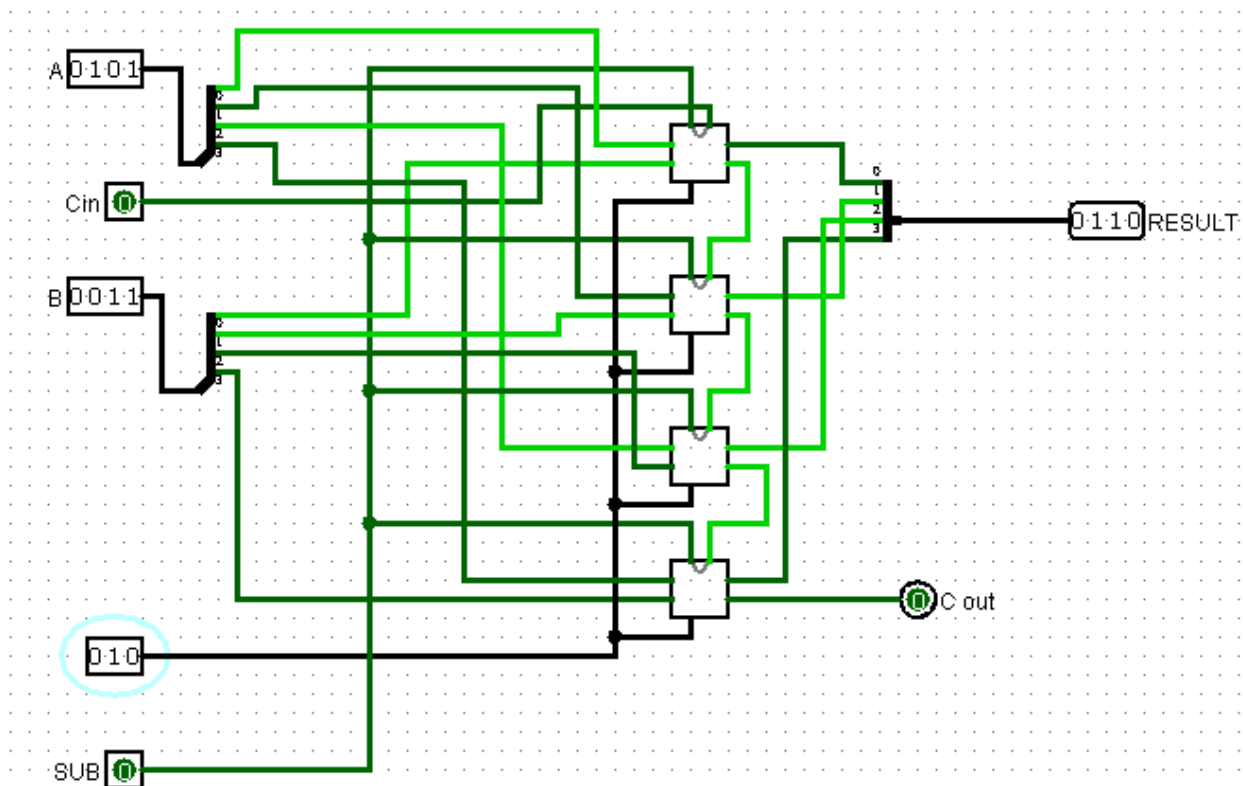

- Initially, we set the input of A and B as '0101' and '0011' respectively. The 4-bit ALU performs the same operations as 1-bit ALU and displays the result in 4-bit binary number.


- On choosing the same select line for XOR Operator as we did in 1-bit ALU i.e., '010', we get the result as '0110'.
- Similarly, we can do this for other operations.

### **AND Operation:**

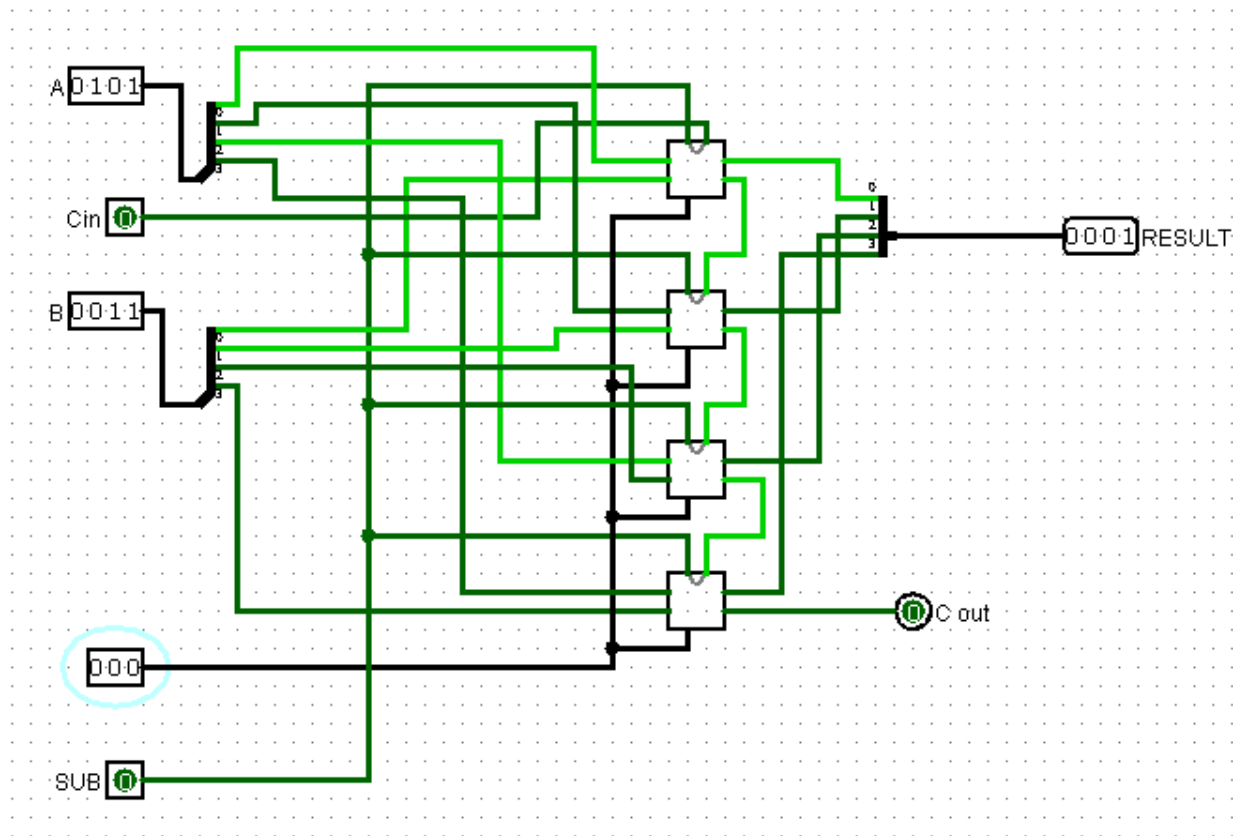




## OR Operation:

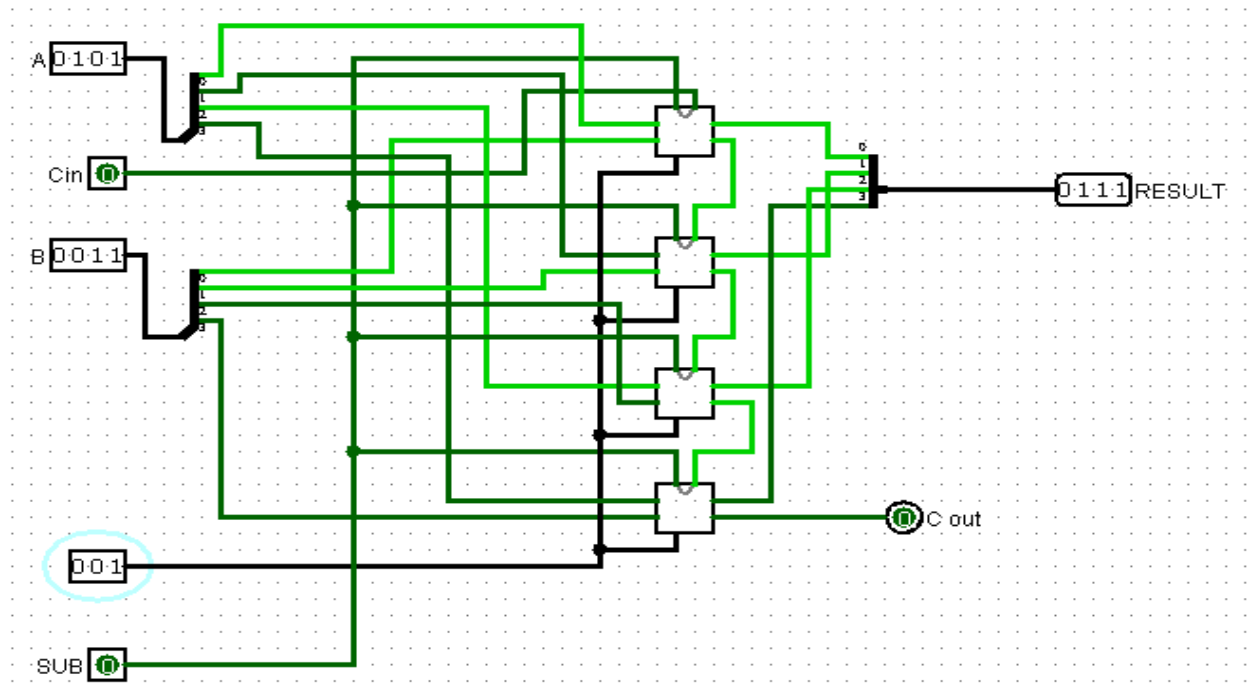


## NOR Operation:

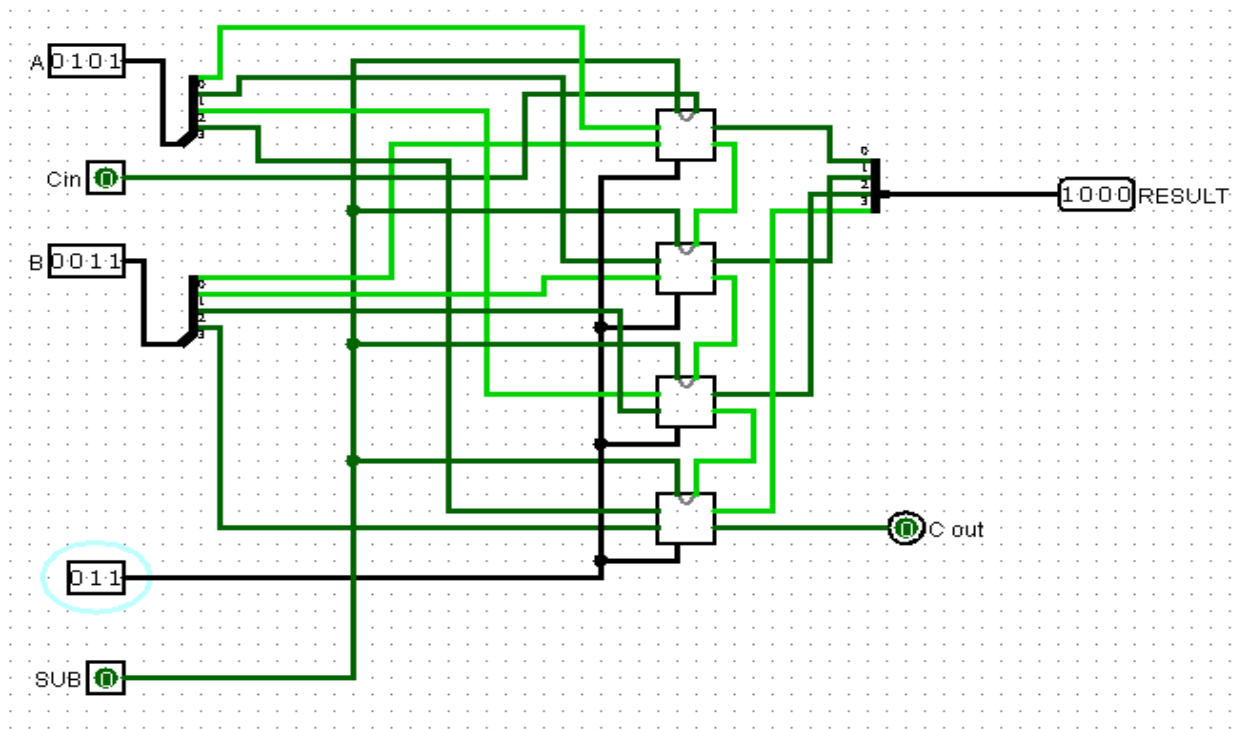


## COMPARATOR Operation:


- Less Than Operation:

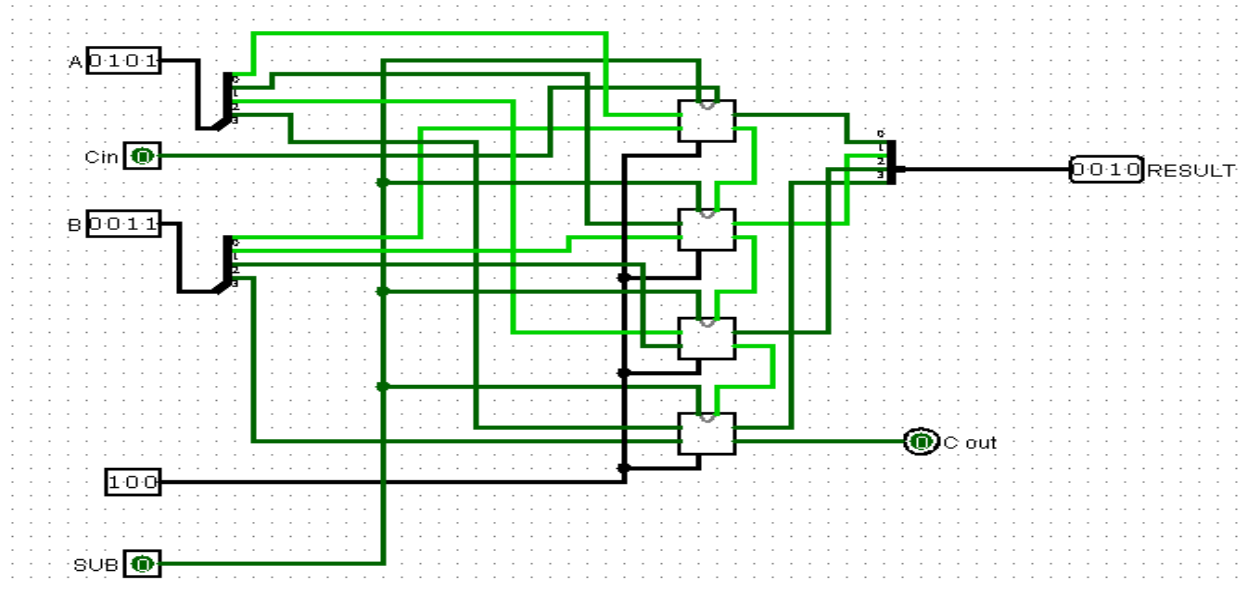

- Equal To Operation:

 


- Greater Than Operation:

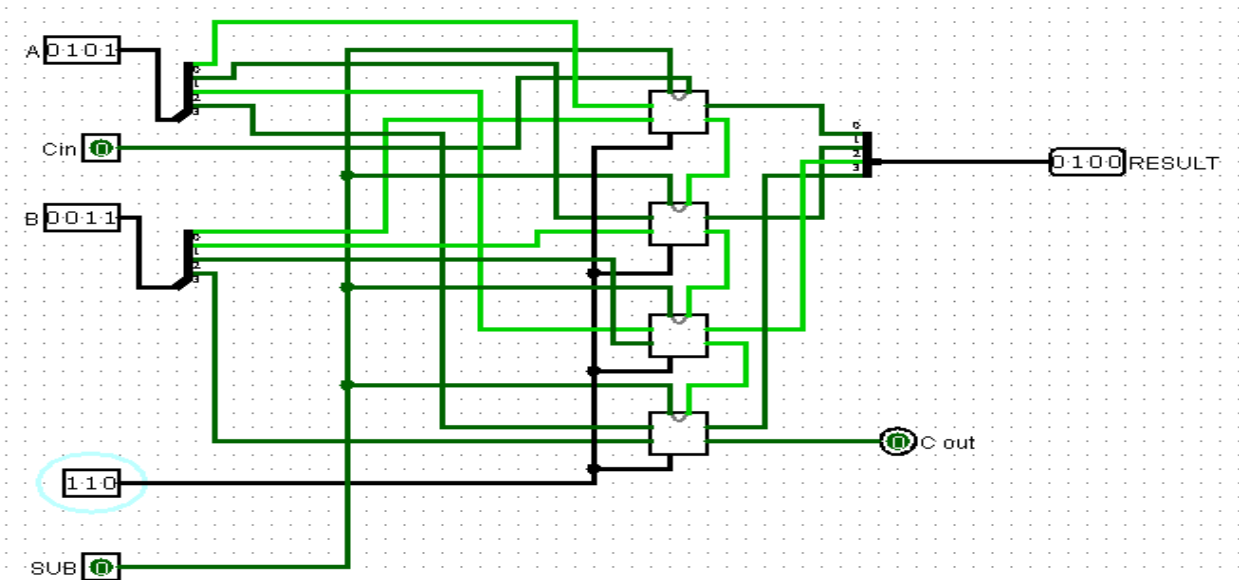


## ADDER Operation:

- Carry Input As 0:

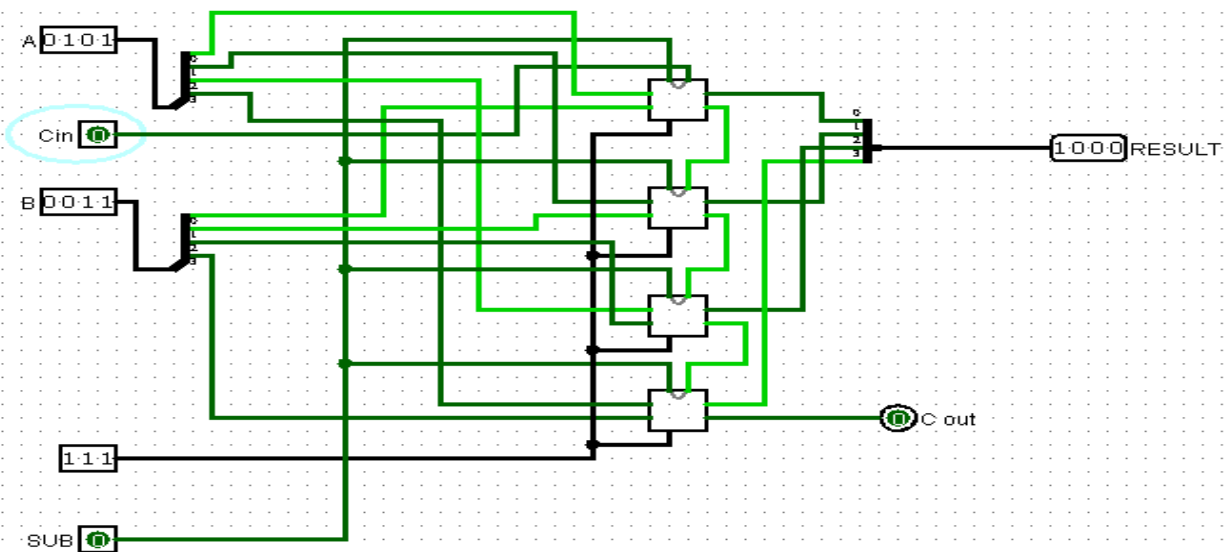


- Carry Input As 1:

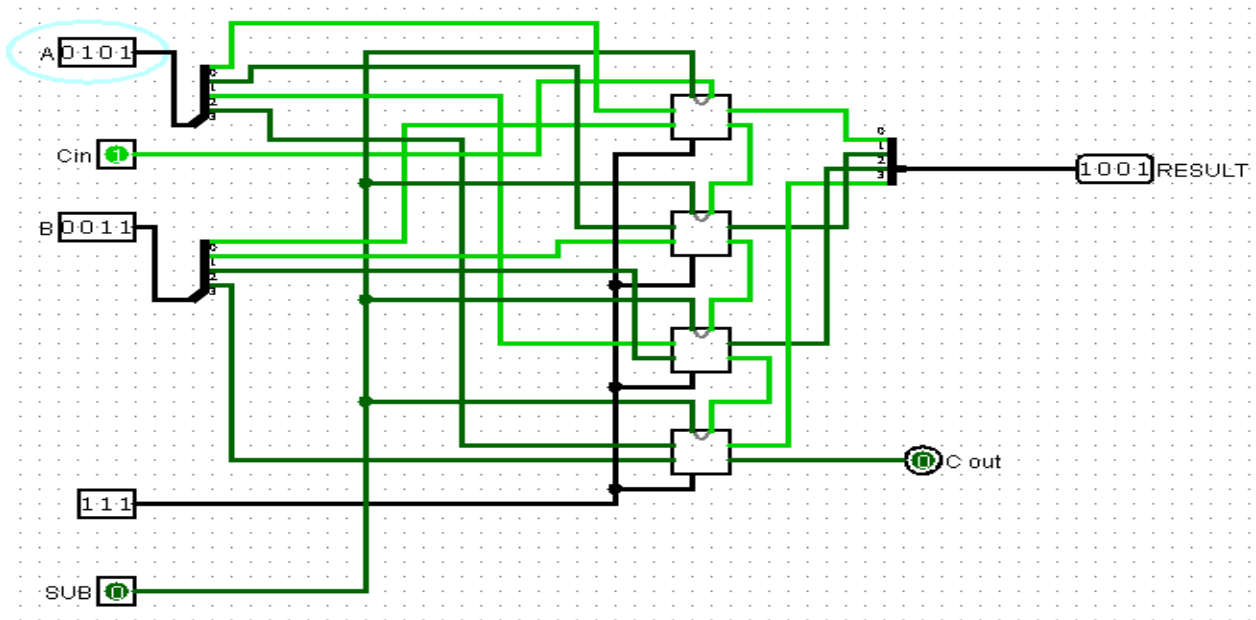


## SUBTRACTOR Operation:

- Sub Input As 1:

 

# CS - 268 | Lab Report

 


## Report File | Week - 02

## Question:

To implement Data Path Architecture structure using 4-bit ALU
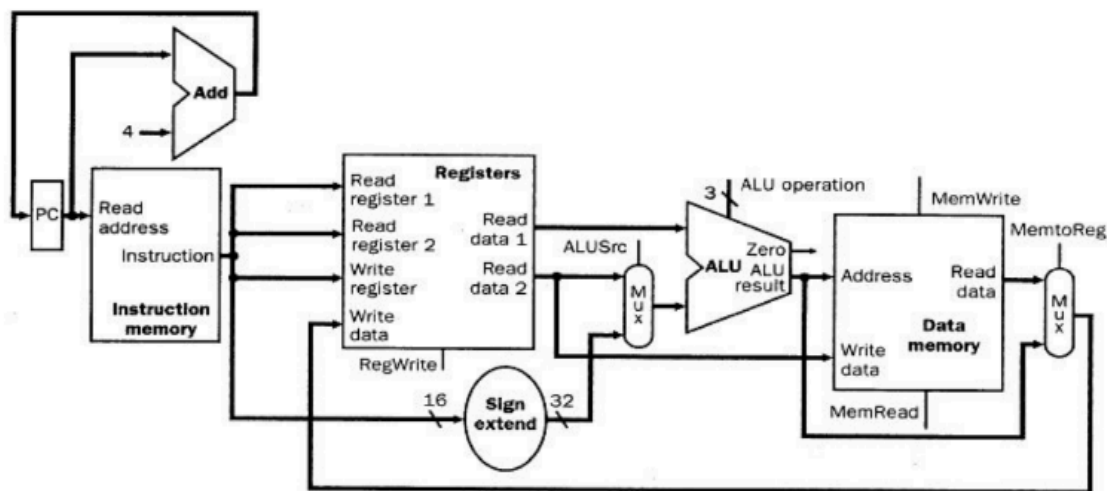
## Theory & Design:


- ❖ A data path (also written as datapath) is a set of functional units that carry out data processing operations.
- ❖ Datapaths, along with a control unit, make up the CPU (central processing unit) of a computer system.
- ❖ A larger data path can also be created by joining more than one together using multiplexers.
- ❖ Currently, data paths can only be configured once. Researchers are trying to find ways to imprint data paths on fabrics and make them reconfigurable.
- ❖ This action would allow them to be configured at runtime, providing for improved efficiency and power savings.



## **Test & Output:**



# CS - 268 | Lab Report

 

## Report File | Week - 03

**Aim:**

# Design and implementation of Booth Multiplier in Verilog

## Objective:

- To find the error in BoothMultiplier.v file
- To ensure the proper working of BoothMultiplier
- To ensure that proper state are activated with respect to q0 and qm1

In this experiment we (202251069)Malaika Varshney, (202251096)Pradumya Gorav and (202251095)Sourabh Patil have analyzed the code part and found 4 errors.

```
module boothmultiplier
(
  LdA, LdQ, LdM, clrA, clrQ, clrff, sftA, sftQ, addsub, ldcnt, data_in, decr, clk, q0, qm1, eqz
); //
  objective M*Q Datapath

  input LdA, LdQ, LdM, clrA, clrQ, clrff, sftA, sftQ, addsub, ldcnt, decr, clk;

  input [15:0] data_in;

  output q0, qm1, eqz;

  wire temp;

  wire [15:0] A, Q, M, Z;

  wire [5:0] count;

  assign eqz = ~|count;

  shiftreg AR(LdA, clrA, Z, sftA, A, clk, A[15]); //Submodule for accumulator

  shiftreg QR(LdQ, clrQ, data_in, sftQ, Q, clk, A[0]); //Submodule for multiplier
```

```

    dff QM1(Q[0],q0,clk,clrff); //Submodule for buffer

    dff Q0(q0,qm1,clk,clrff);

    addsum AS(Z,A,M,addsub); //Submodule for adder

    PIPO MR(LdM,data_in,M,clk); //Submodule for Multiplicand

    CNTR CN(ldcnt,clk,decr,count); //Submodule for counter

endmodule

// To make the ASR shift

module shiftreg (ld,clr,din,sft,dout,clk,s_in);

    input ld,clr,sft,clk,s_in;

    output reg [15:0] dout;

    input [15:0] din;

    always@(posedge clk) //clock Shift register A & Q
        begin
            if(clr)
                dout<=0;

            else if (ld)
                dout<=din;

            else if (sft)
                dout<={s_in,dout[15:1]};

        end

endmodule

// To load multiplier

module PIPO(ld,din,dout,clk);

```

```

    input[15:0] din;

    input ld,clk;

    output reg [15:0] dout;

    always@(posedge clk) //clock for register M

        if (ld)

            dout<=din;

endmodule

// To load q0,qm1

module dff(d,q,clk,clr);

    input clr,clk,d;

    output reg q;

    always@(posedge clk) // clock for buffer register

        if (clr)

            #1 q<=0;

        else

            #1 q<=d;

endmodule

// To make AC=AC+M OR AC=AC-M

module addsum(out,in1,in2,addsub);

    input[15:0] in1,in2;

    input addsub;

    output reg[15:0] out;

    always@(*)

        begin

```

```

        if (addsub==0)

            out=in1-in2;

        else

            out=in1+in2;

        end

    endmodule

// To make a counter for clock

module CNTR (ldcnt,clk,decr,count);

    input ldcnt,decr,clk;

    output reg[5:0] count;

    always@(posedge clk) // clock for counter

        begin

            if (ldcnt)

                count=5'b10000;

            else if(decr)

                count<=count-1;

        end

endmodule

// To check state

module controller

(LdA,LdQ,LdM,clrA,clrQ,clrff,sftA,sftQ,addsub,ldcnt,decr,done,clk,Q0,qm1,eqz,start); //
control path code

    input clk,Q0,qm1,eqz,start;

    output reg LdA,LdQ,LdM,clrA,clrQ,clrff,sftA,sftQ,addsub,ldcnt,decr,done;

    reg[2:0] state;

```

```

parameter s0=3'b000,s1=3'b001,s2=3'b010,s3=3'b011,s4=3'b100,s5=3'b101,s6=3'b110;

always @(posedge clk)

    begin

        case(state)

            s0: if(start) state<=s1;

            s1: #2 state<=s2;

            s2: if(({Q0,qm1}==2'b01) state<=s3;

                    else if(({Q0,qm1}==2'b10) state<=s4;

                    else state<=s5;

            s3: state<=s5;

            s4: state<=s5;

            s5: #2 if (({Q0,qm1}==2'b01) && !eqz) state<=s3;

                    else if (({Q0,qm1}==2'b10) && !eqz) state<=s4;

                    else if(eqz) state<=s6;

            s6: state<=s6;

            default: state <=s0;

        endcase

    end

always@(state)

    begin

        case(state)

            s0: begin
LdA=0;clrA=0;sftA=0;LdQ=0;clrQ=0;clrff=1;LdQ=0;sftQ=0;LdM=0;done=0;end

            s1: begin clrA=1;clrff=0;ldcnt=1;LdQ=1;end

            s2: begin clrA=0;clrff=0;ldcnt=0;LdM=1;LdQ=0;end

            s3: begin LdA=1;addsub=1;LdQ=0;sftA=0;sftQ=0;decr=0;end

            s4: begin LdA=1;LdQ=0;sftA=0;sftQ=0;decr=0;addsub=0;end

```

```

s5: begin LdA=0;sftA=1;LdQ=0;sftQ=1;decr=1;end

s6: done=1;

default: begin LdA=0;clrA=0;LdQ=0;clrQ=0;clrff=0;LdM=0;end

        endcase

    end

endmodule

```

## Test Bench:

```

module BoothMultiplier_tb();

    reg [15:0] data_in;

    reg clk,start;

    wire done;

    boothmultiplier BM
(LdA,LdQ,LdM,clrA,clrQ,clrff,sftA,sftQ,addsub,ldcnt,data_in,decr,clk,q0,qm1,eqz);

    controller
CL(LdA,LdQ,LdM,clrA,clrQ,clrff,sftA,sftQ,addsub,ldcnt,decr,done,clk,q0,qm1,eqz,start);

    initial

        begin

            $monitor("Time Q A state");

            clk=0;

            start=1;

        end

    always #5 clk=~clk;

    initial

        begin

            # 10 data_in=3;

```





```


225000000000000001010 0000000000000000 6 1
23500000000000000101 0000000000000000 6 1
24500000000000000010 0000000000000000 6 1
.\BoothMultiplier_tb.v:28: $finish called at 250 (1s)
PS D:\IMPORTANT\SEM-4\LAB\CS268\Lab_03> gtkwave test_booth.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[250] end time.

```


## Gtkwave:

 

## Conclusion:



# CS - 268 | Lab Report

 

## Report File | Week - 04

## **Aim:**

Design and implementation of memory in Verilog

## **Objective:**

- Design & simulate a memory which has a 5 bit address line and 32 bit data line, the given memory has two read ports & one write port. It is mandatory to use the positive edge of the clock pulse to write data in the memory but the reading of data from memory has no such condition.
- It is recommended to use continuous assignment for reading the data from memory and procedural assignment for writing the data in memory.

In this experiment we (202251069)Malaika Varshney, (202251096)Pradumya Gorav and (202251095)Sourabh Patil have analyzed the code part and created a testbench in this experiment.

```

module regbank_v4 (

    rdData1,rdData2,wrData,sr1,sr2,dr,write,reset,clk);

    input clk,write,reset;

    input [4:0] sr1,sr2,dr;

    input [31:0] wrData;

    output [31:0] rdData1,rdData2;

    integer k;

    output reg [31:0] regfile[0:31];

    always @(posedge clk ) begin

        begin

            if (reset) begin

                for (k =0 ;k<32 ;k=k+1 ) begin

                    regfile[k] <= 0;

                end

            end

            else if (write) begin

                regfile[dr] <= wrData;

            end

        end

        end

        assign rdData1=regfile[sr1];

        assign rdData2=regfile[sr2];

    endmodule

```

# Test Bench:

```
module regbank_v4_tb();

    reg clk,write,reset;

    reg [4:0] sr1,sr2,dr;

    reg [31:0] wrData;

    wire [31:0] rdData1,rdData2;

    wire [31:0] regfile[31:0];

    integer k;

    regbank_v4 uut(rdData1,rdData2,wrData,sr1,sr2,dr,write,reset,clk);

    always #5 clk=~clk;

    initial begin

        clk=0;

        $dumpfile("test.vcd");

        $dumpvars(0,regbank_v4_tb);

        #7 reset=1;

        #10 reset=0;

        for (k = 0;k<32 ;k=k+1 ) begin

            #5

            write=1;

            dr=k;

            wrData=10*k+1;

            #5 write=0;

        end

    end
```



```

        for (k =0 ;k<32 ;k=k+2) begin

            #5

            srl=k;

            sr2=k+1;

            $monitor("%d %d",rdData1,rdData2) ;

            $dumpvars (regfile[k]) ;

        end

        $finish() ;

    end

endmodule

```

## Terminal:

```

PS D:\IMPORTANT\SEM-4\LAB\CS268\Lab_04> iverilog -o test .\lab_04_c.v
.\lab_04_c_tb.v
PS D:\IMPORTANT\SEM-4\LAB\CS268\Lab_04> vvp test
VCD info: dumpfile test.vcd opened for output.
rdData1=      1 rdData2=      11
rdData1=     21 rdData2=     31
rdData1=     41 rdData2=     51
rdData1=     61 rdData2=     71
rdData1=     81 rdData2=     91
rdData1=    101 rdData2=    111
rdData1=    121 rdData2=    131
rdData1=    141 rdData2=    151
rdData1=    161 rdData2=    171
rdData1=    181 rdData2=    191
rdData1=    201 rdData2=    211
rdData1=    221 rdData2=    231
rdData1=    241 rdData2=    251
rdData1=    261 rdData2=    271
rdData1=    281 rdData2=    291
.\lab_04_c_tb.v:33: $finish called at 417 (1s)
rdData1=    301 rdData2=    311

```




```
PS D:\IMPORTANT\SEM-4\LAB\CS268\Lab_04> gtkwave .\test.vcd
```

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.

[417] end time.

## Gtkwave:

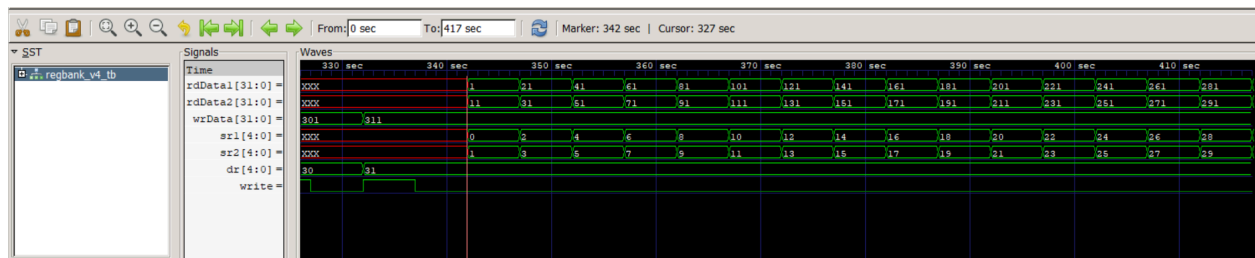  


## Conclusion:

- The clock signal toggles every 5 time units.
- The reset signal transitions from 2'b00 to 2'b01 to 2'b10 at time intervals of 5 time units.
- The state machine transitions through s0, s1, and s2 in response to the clock signal.

Within GTKWave, it is possible to view waveforms depicting signals like clock, reset, and light. The patterns displayed should demonstrate the state machine cyclically transitioning through its states, potentially with an initial reset. The light signal's waveform is expected to mirror the color corresponding to each state.

# CS - 268 | Lab Report

 

## Report File | Week - 05

## **Aim:**

Design and implementation of pipeline in Verilog

## **Objective:**

- Design & simulate a memory which has a 5 bit address line and 32 bit data line, the given memory has two read ports & one write port. It is mandatory to use the positive edge of the clock pulse to write data in the memory but the reading of data from memory has no such condition.
- It is recommended to use continuous assignment for reading the data from memory and procedural assignment for writing the data in memory.

In this experiment we (202251069)Malaika Varshney, (202251096)Pradumya Gorav and (202251095)Sourabh Patil have analyzed the code part and created a testbench in this experiment.

```
module pipe_ex (
    F,A,B,C,D,clk
);

parameter N = 10;

input [N-1:0] A,B,C,D;

input clk;

output [N-1:0] F;

reg [N-1:0] L12_x1,L12_x2,L12_D,L23_x3,L23_D,L34_F;

assign F=L34_F;

always @(posedge clk )

begin

    L12_x1 <= #4A+B;

    L12_x2 <= #4C-D;

    L12_D  <=D;

    L23_x3 <= #4L12_x1+L12_x2;

    L23_D  <=L12_D;

    L34_F  <= #6L23_x3*L23_D;

end

endmodule
```

# Test Bench:

```
module pip_tb();

    parameter N = 10;

    reg [N-1:0] A,B,C,D;

    reg clk;

    wire [N-1:0] F;

    pipe_ex uut (F,A,B,C,D,clk);

    always #10 clk = ~clk;

    initial begin

        $dumpfile("pip_tb.vcd");

        $dumpvars(0,pip_tb);

        clk=1;

        A=2;B=3;C=5;D=4;

        $monitor("A=%d B=%d C=%d D=%d F=%d",A,B,C,D,F);

        #10;

        A=6;B=7;C=9;D=9;

        $monitor("A=%d B=%d C=%d D=%d F=%d",A,B,C,D,F);

        #10;

        A=10;B=11;C=13;D=13;

        $monitor("A=%d B=%d C=%d D=%d F=%d",A,B,C,D,F);

        #10;

        A=14;B=15;C=17;D=17;

        $monitor("A=%d B=%d C=%d D=%d F=%d",A,B,C,D,F);
```



```

        #100;

        $finish();

    end

endmodule

```

## Terminal:

```


PS D:\IMPORTANT\SEM-4\LAB\CS268\Lab_05> iverilog -o test .\pip.v pip_tb.v
PS D:\IMPORTANT\SEM-4\LAB\CS268\Lab_05> vvp test
VCD info: dumpfile pip_tb.vcd opened for output.
A=  2 B=  3 C=  5 D=  4 F=  x
A=  6 B=  7 C=  9 D=  9 F=  x
A= 10 B= 11 C= 13 D= 13 F=  x
A= 10 B= 11 C= 13 D= 13 F= 24
A= 14 B= 15 C= 17 D= 17 F= 24
A= 14 B= 15 C= 17 D= 17 F= 117
A= 14 B= 15 C= 17 D= 17 F= 273
A= 14 B= 15 C= 17 D= 17 F= 493
pip_tb.v:27: $finish called at 130 (1s)
PS D:\IMPORTANT\SEM-4\LAB\CS268\Lab_05> gtkwave .\pip_tb.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[130] end time.

```

## Gtkwave:

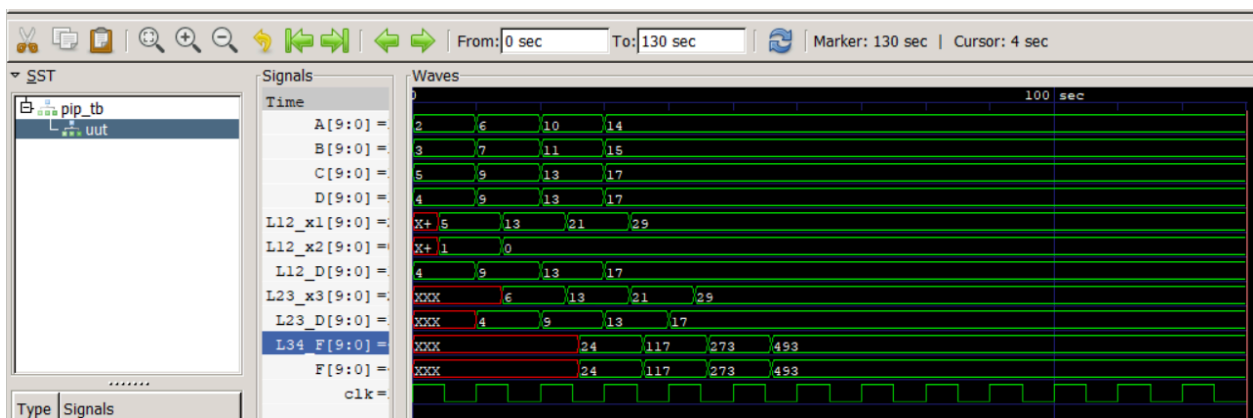

## **Conclusion:**

- The clock signal toggles every 5 time units.
- The reset signal transitions from 2'b00 to 2'b01 to 2'b10 at time intervals of 5 time units.
- The state machine transitions through s0, s1, and s2 in response to the clock signal.

Within GTKWave, it is possible to view waveforms depicting signals like clock, reset, and light. The patterns displayed should demonstrate the state machine cyclically transitioning through its states, potentially with an initial reset. The light signal's waveform is expected to mirror the color corresponding to each state.

**CS-268**

**MID-SEM REPORT FILE COMPLETED**

**THANK YOU**